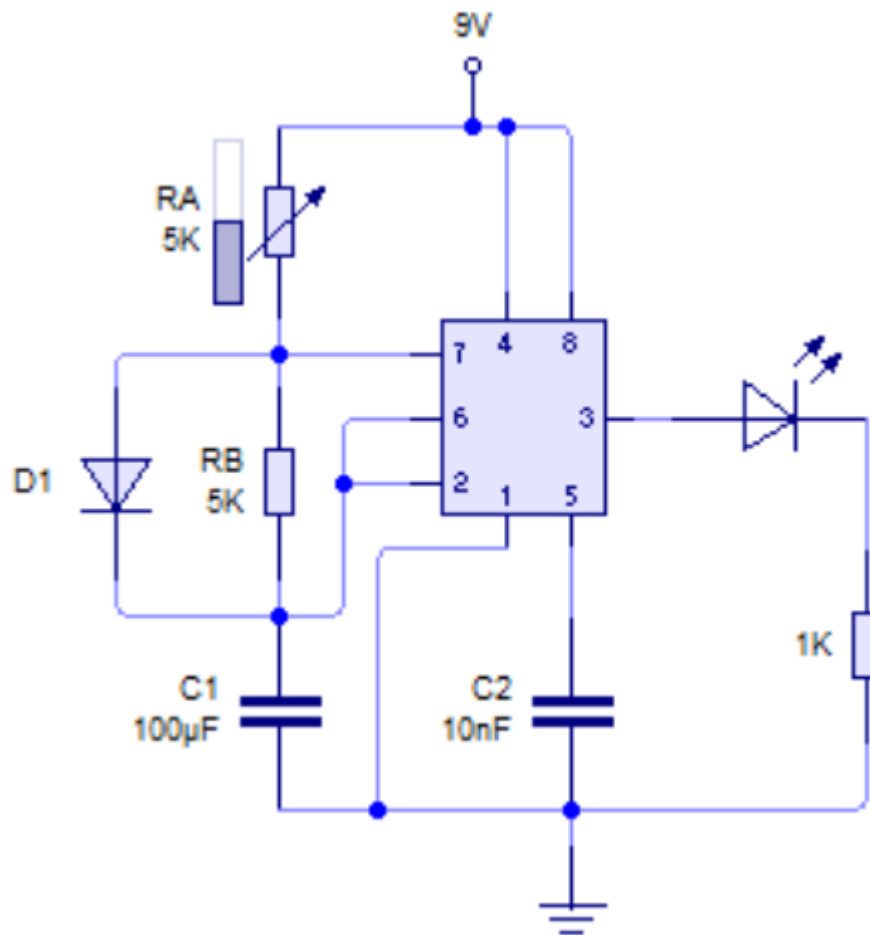


555:



Tiempos:

$$T_{ON} = 0,693 \cdot R_A \cdot C_1$$

$$T_{OFF} = 0,693 \cdot R_B \cdot C_1$$

Duty:

$$D = \frac{R_A}{R_A + R_B}$$

Para duty = 50%; $R_A = R_B$

$$T_{ON} = 0.693 \cdot 1.5k\Omega \cdot 10\mu F = 10.395 \text{ ms}$$

$$T_{off} = 0.693 * 1.5k\Omega * 10\mu F = 10.395 \text{ mS}$$

$$T = 10.395 \text{ mS} + 10.395 \text{ mS} = 20.79 \text{ mS}$$

$$f = 48.1 \text{ Hz}$$

Referencias:

https://www.electronics-tutorials.ws/waveforms/555_oscillator.html